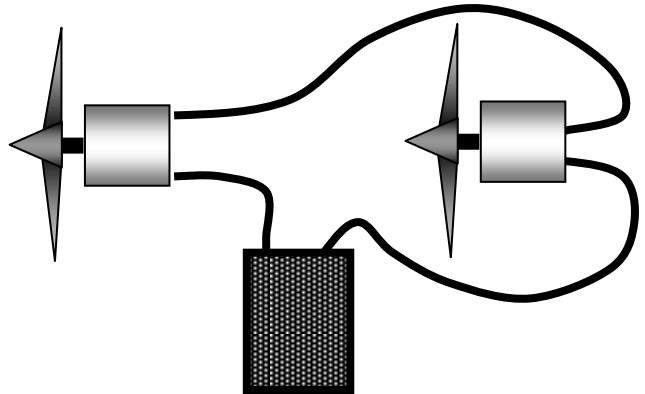


## Series Parallel Circuits

### Series


Explain the series circuit drawn to the right.



Observations
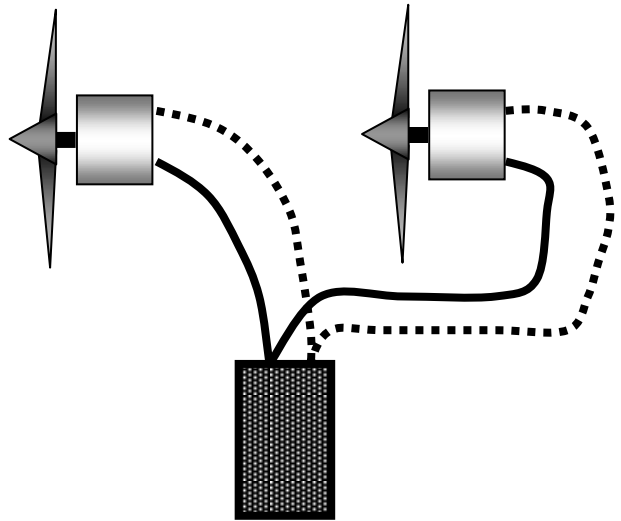
### Parallel

Explain the parallel circuit drawn to the right.



Observations

Which circuit would you use to wire your hovercraft? Why?